



SWE223: Digital Electronics Fall 2015



Lecture 3
Tanjila Farah (TF)

Textbooks

- ▶ Moris Mano and Kime, “Logic & Computer Design Fundamentals”, Prentice Hall.






Theorems and Postulates




LOGIC CIRCUIT DESIGN

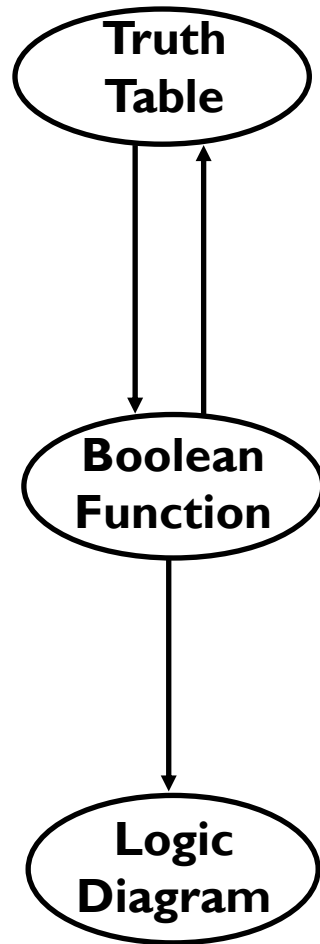

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$F = x + y'z$

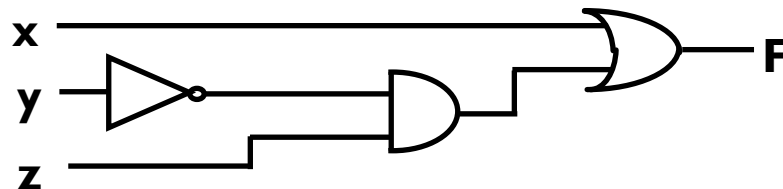

Boolean Algebra

Boolean identities

Name	AND version	OR version
Identity	$x \cdot 1 = x$	$x + 0 = x$
Complement	$x \cdot \overline{x} = 0$	$x + \overline{x} = 1$
Commutative	$x \cdot y = y \cdot x$	$x + y = y + x$
Distribution	$x \cdot (y + z) = xy + xz$	$x + (y \cdot z) =$ $(x + y) (x + z)$
Idempotent	$x \cdot x = x$	$x + x = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$

Boolean Algebra (cont.)

Name	AND version	OR version
Involution	$\overline{\overline{x}} = x$	$---$
Absorption	$x \cdot (x + y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) =$ $(x + y) + z$
de Morgan	$\overline{x \cdot y} = \overline{x} + \overline{y}$	$\overline{x + y} = \overline{x} \cdot \overline{y}$



Identifying postulates and theorems

▶ **Basic Postulates**

- ▶ **Postulate 1 (Definition):** A Boolean algebra is a closed algebraic system containing a set K of two or more elements and the two operators \bullet and $+$.

- ▶ **Postulate 2 (Existence of 1 and 0 element):**

(a) $a + 0 = a$ (identity for $+$), (b) $a \bullet 1 = a$ (identity for \bullet)

- ▶ **Postulate 3 (Commutativity):**

(a) $a + b = b + a$, (b) $a \bullet b = b \bullet a$

- ▶ **Postulate 4 (Associativity):**

(a) $a + (b + c) = (a + b) + c$ (b) $a \bullet (b \bullet c) = (a \bullet b) \bullet c$

- ▶ **Postulate 5 (Distributivity):**

(a) $a + (b \bullet c) = (a + b) \bullet (a + c)$ (b) $a \bullet (b + c) = a \bullet b + a \bullet c$

- ▶ **Postulate 6 (Existence of complement):**

(a) $a + \bar{a} = 1$ (b) $a \bullet \bar{a} = 0$

- ▶ Normally \bullet is omitted.



Identifying postulates and theorems (cont')

▶ **Fundamental Theorems of Boolean Algebra**

▶ **Theorem 1 (Idempotency):**

$$(a) \ a + a = a$$

$$(b) \ aa = a$$

▶ **Theorem 2 (Null element):**

$$(a) \ a + 1 = 1$$

$$(b) \ a0 = 0$$

▶ **Theorem 3 (Involution)**

$$\overline{\overline{a}} = a$$

▶ **Theorem 4 (Absorption)**

$$(a) \ a + ab = a$$

$$(b) \ a(a + b) = a$$

▶ **Examples:**

$$\blacktriangleright \ (X + Y) + (X + Y)Z = X + Y \quad [T4(a)]$$

$$\blacktriangleright \ AB'(AB' + B'C) = AB' \quad [T4(b)]$$

▶ **Theorem 5**

$$\blacktriangleright \ (a) \ a + a'b = a + b$$

$$(b) \ a(a' + b) = ab$$

Identifying postulates and theorems (cont')

► **Fundamental Theorems of Boolean Algebra**

► **Examples:**

► $B + AB'C'D = B + AC'D$ [T5(a)]

► $(X + Y)((X + Y)' + Z) = (X + Y)Z$ [T5(b)]

► **Theorem 6**

(a) $ab + ab' = a$

(b) $(a + b)(a + b') = a$

► **Examples:**

► $ABC + AB'C = AC$ [T6(a)]

► $(W' + X' + Y' + Z')(W' + X' + Y' + Z)(W' + X' + Y + Z')(W' + X' + Y + Z)$

$= (W' + X' + Y')(W' + X' + Y + Z')(W' + X' + Y + Z)$

[T6(b)]

$= (W' + X' + Y')(W' + X' + Y)$

[T6(b)]

$= (W' + X')$

[T6(b)]



Fundamentals of Boolean Algebra (5)

► **Theorem 7**

$$(a) \quad ab + ab'c = ab + ac + b)(a + c)$$

$$(b) \quad (a + b)(a + b' + c) = (a$$

► **Examples:**

$$\begin{aligned} \blacktriangleright \quad wy' + wx'y + wxyz + wxz' &= wy' + wx'y + wxy + wxz' \\ &\quad [T7(a)] \\ &= wy' + wy + wxz' \\ &\quad [T7(a)] \\ &= w + wxz' \quad [T7(a)] \\ &= w \quad [T7(a)] \\ \blacktriangleright \quad (x'y' + z)(w + x'y' + z') &= (x'y' + z)(w + x'y') \quad [T7(b)] \end{aligned}$$



Fundamentals of Boolean Algebra (6)

▶ **Theorem 8 (DeMorgan's Theorem)**

$$(a) \quad (a + b)' = a'b'$$

$$(b) \quad (ab)' = a' + b'$$

▶ Generalized DeMorgan's Theorem

$$(a) \quad (a + b + \dots + z)' = a'b' \dots z'$$

$$(b) \quad (ab \dots z)' = a' + b' + \dots$$

▶ **Examples:**

$$\begin{aligned} \blacktriangleright \quad (a + bc)' &= (a + (bc))' && [T8(a)] \\ &= a'(bc)' && [T8(b)] \\ &= a'(b' + c') && [P5(b)] \\ &= a'b' + a'c' \end{aligned}$$

$$\blacktriangleright \quad \text{Note: } (a + bc)' \neq a'b' + c'$$



Fundamentals of Boolean Algebra (7)

► **More Examples for DeMorgan's Theorem**

$$\begin{aligned}\text{► } (a(b + z(x + a')))' &= a' + (b + z(x + a'))' && [\text{T8(b)}] \\ &= a' + b' (z(x + a'))' && [\text{T8(a)}] \\ &= a' + b' (z' + (x + a'))' && [\text{T8(b)}] \\ &= a' + b' (z' + x'(a'))' && [\text{T8(a)}] \\ &= a' + b' (z' + x'a) && [\text{T3}] \\ &= a' + b' (z' + x') && [\text{T5(a)}]\end{aligned}$$

$$\begin{aligned}\text{► } (a(b + c) + a'b)' &= (ab + ac + a'b)' && [\text{P5(b)}] \\ &= (b + ac)' && [\text{T6(a)}] \\ &= b'(ac)' && [\text{T8(a)}] \\ &= b'(a' + c') && [\text{T8(b)}]\end{aligned}$$



DeMorgan's: Example

Solution

$$F_2 = \overline{(\overline{X} + Z)(\overline{XY})}$$

$$F_2 = \overline{(\overline{X} + Z)} + \overline{(\overline{XY})} \quad ; \text{Theorem \#14A}$$

$$F_2 = (\overline{\overline{X} + Z}) + (XY) \quad ; \text{Theorem \#9}$$

$$F_2 = (\overline{\overline{X}} \overline{\overline{Z}}) + (XY) \quad ; \text{Theorem \#14B}$$

$$F_2 = (X \overline{Z}) + (XY) \quad ; \text{Theorem \#9}$$

$$F_2 = X \overline{Z} + X Y \quad ; \text{Rewritten without AND symbols}$$



Fundamentals of Boolean Algebra (8)

▶ **Theorem 9 (Consensus)**

$$(a) \quad ab + a'c + bc = ab + a'c \quad (b) \quad (a + b)(a' + c)(b + c) = (a + b)(a' + c)$$

▶ **Examples:**

$$\blacktriangleright \quad AB + A'CD + BCD = AB + A'CD \quad [T9(a)]$$

$$\blacktriangleright \quad (a + b')(a' + c)(b' + c) = (a + b')(a' + c) \quad [T9(b)]$$

$$\blacktriangleright \quad ABC + A'D + B'D + CD = ABC + (A' + B')D + CD \quad [P5(b)]$$

$$= ABC + (AB)'D + CD \quad [T8(b)]$$

$$= ABC + (AB)'D \quad [T9(a)]$$

$$= ABC + (A' + B')D$$

$$[T8(b)]$$

$$= ABC + A'D + B'D$$

$$[P5(b)]$$



Boolean Algebra (cont.)

▶ **Usefulness of these Tables**

- **Simplification of the Boolean function**
- **Derivation of equivalent Boolean functions to obtain logic diagrams utilizing different**





K-MAP



Algebraic Forms

- ▶ **Literal:** A variable, complemented or uncomplemented.
- ▶ **Product term:** A literal or literals ANDed together.
- ▶ **Sum term:** A literal or literals ORed together.

- ▶ **SOP (Sum of Products):**
 - ▶ ORing product terms
 - ▶ $f(A, B, C) = ABC + A'C + B'C$

- ▶ **POS (Product of Sums)**
 - ▶ ANDing sum terms
 - ▶ $f(A, B, C) = (A' + B' + C')(A + C')(B + C')$



Algebraic Forms cont'

- ▶ A **minterm** is a product term in which all the variables appear exactly once either complemented or uncomplemented.
- ▶ **Canonical Sum of Products (canonical SOP):**
 - ▶ Represented as a sum of minterms only.
 - ▶ **Example:** $f_1(A,B,C) = A'BC' + ABC' + A'BC + ABC$
- ▶ Minterms of three variables:

Minterm	Minterm Code	Minterm Number
$A'B'C'$	000	m_0
$A'B'C$	001	m_1
$A'BC'$	010	m_2
$A'BC$	011	m_3
$AB'C'$	100	m_4
$AB'C$	101	m_5
ABC'	110	m_6
ABC	111	m_7



Algebraic Forms cont'


- ▶ A **maxterm** is a sum term in which all the variables appear exactly once either complemented or uncomplemented.
- ▶ **Canonical Product of Sums (canonical POS):**
 - ▶ Represented as a product of maxterms only.
 - ▶ **Example:** $f_2(A,B,C) = (A+B+C)(A+B+C')(A'+B+C)(A'+B+C')$ (2.7)
- ▶ Maxterms of three variables:

Maxterm	Maxterm Code	Maxterm Number
$A+B+C$	000	M_0
$A+B+C'$	001	M_1
$A+B'+C$	010	M_2
$A+B'+C'$	011	M_3
$A'+B+C$	100	M_4
$A'+B+C'$	101	M_5
$A'+B'+C$	110	M_6
$A'+B'+C'$	111	M_7



KARNAUGH MAP

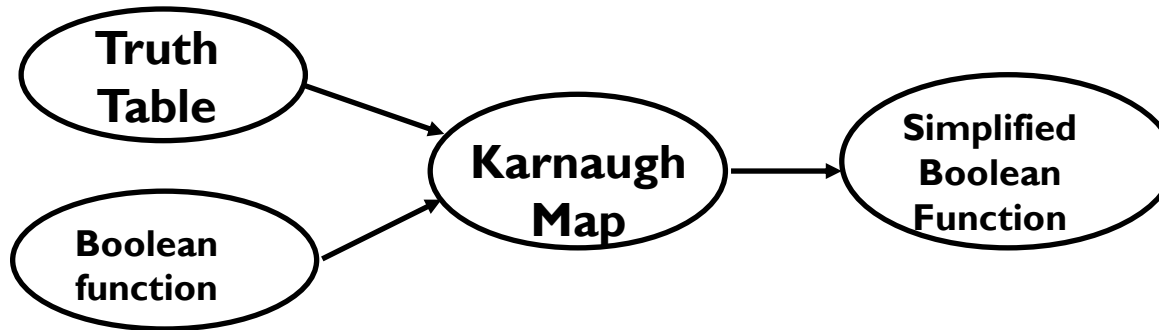- ▶ **Karnaugh Map (K-map)** is a simple procedure for simplifying **Boolean expressions**.




- ▶ **Karnaugh Map for an n-input digital logic circuit (n-variable sum-of-products form of Boolean Function, or Truth Table) is**
 - ▶ - Rectangle divided into 2^n cells
 - ▶ - Each cell is associated with a *Minterm*
 - ▶ - An output(function) value for each input value associated with a minterm is written in the cell representing the minterm
 - ▶ → 1-cell, 0-cell
 - ▶ **Each Minterm is identified by a decimal number whose binary representation is identical to the binary interpretation of the input values of the minterm.**
-




KARNAUGH MAP cont'

x	F
0	1
1	0

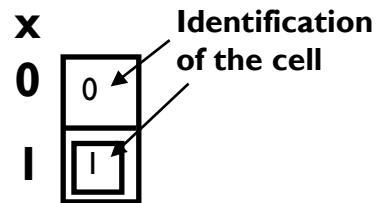



Karnaugh Map

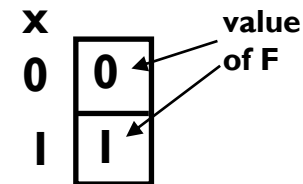

$$F(x) = \sum (1)$$

↑
1-cell

x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

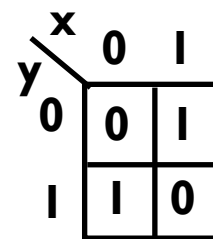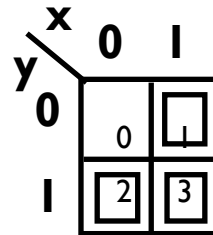

$$F(x,y) = \sum (1,2)$$



KARNAUGH MAP cont'

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

		yz			
		00	01	11	10
x	0	0	1	3	2
	1	4	5	7	6

		yz			
		00	01	11	10
x	0	0	1	0	1
	1	1	0	0	0

$$F(x,y,z) = \sum (1,2,4)$$

u	v	w	x	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

		wx			
		00	01	11	10
uv	00	0	1	3	2
	01	4	5	7	6
u	11	12	13	15	14
	10	8	9	11	10

		wx			
		00	01	11	10
uv	00	0	1	1	0
	01	0	0	0	1
u	11	0	0	0	1
	10	1	1	1	0

$$F(u,v,w,x) = \sum (1,3,6,8,9,11,14)$$



MAP SIMPLIFICATION - 2 ADJACENT CELLS

Adjacent cells

$$\text{Rule: } xy' + xy = x(y + y') = x$$

- binary identifications are different in one bit
→ minterms associated with the adjacent cells have one variable complemented each other

Cells (1,0) and (1,1) are adjacent

Minterms for (1,0) and (1,1) are

$$x \cdot y' \rightarrow x=1, y=0$$

$$x \cdot y \rightarrow x=1, y=1$$

$F = xy' + xy$ can be reduced to $F = x$

From the map

	y	0	1
x	0	0	0
	1	1	1

2 adjacent cells xy' and xy

→ merge them to a larger cell x



$$F(x,y) = \sum (2,3)$$

$$= xy' + xy$$

$$= x$$

MAP SIMPLIFICATION - MORE THAN 2 CELLS
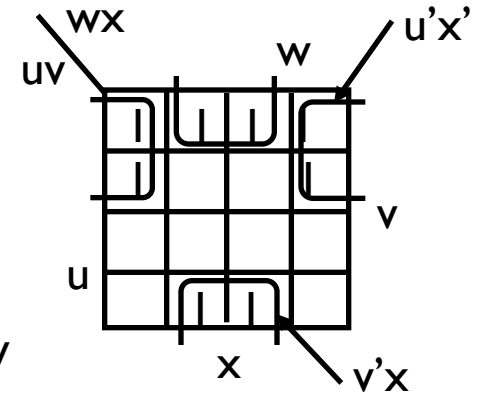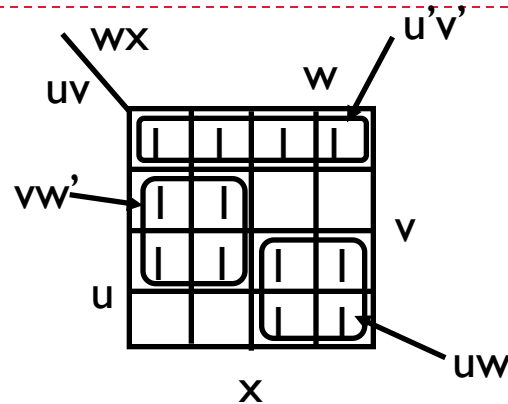
$$\begin{aligned}
 &u'v'w'x' + u'v'w'x + u'v'wx + u'v'wx' \\
 &= u'v'w'(x' + x) + u'v'w(x + x') \\
 &= u'v'w' + u'v'w \\
 &= u'v'(w' + w) \\
 &= u'v'
 \end{aligned}$$



$$\begin{aligned}
 &u'v'w'x' + u'v'w'x + u'vw'x' + u'vw'x + uvw'x' + uvw'x + uv'w'x' + uv'w'x \\
 &= u'v'w'(x' + x) + u'vw'(x' + x) + uvw'(x' + x) + uv'w'(x' + x) \\
 &= u'(v' + v)w' + u(v' + v)w' \\
 &= (u' + u)w' = w'
 \end{aligned}$$

