



# SWE223: Digital Electronics Fall 2015



Lecture 4  
Tanjila Farah (TF)

# Textbooks

---

- ▶ M. Moris Mano “Digital Logic and Computer Design”, Prentice Hall.




# Overview

---

- ▶ Comparator



# Design example: two-bit comparator

 

block diagram  
and  
truth table

A	B	C	D	LT	EQ	GT
0	0	0	0	0	1	0
		0	1	1	0	0
		1	0	1	0	0
		1	1	1	0	0
0	1	0	0	0	0	1
		0	1	0	1	0
		1	0	1	0	0
		1	1	1	0	0
1	0	0	0	0	0	1
		0	1	0	0	1
		1	0	0	1	0
		1	1	1	0	0
1	1	0	0	0	0	1
		0	1	0	0	1
		1	0	0	0	1
		1	1	0	1	0

A			
0	0	0	0
1	0	0	0
1	1	0	1
1	1	0	0
D			
C		B	

K-map for LT

A			
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1
D			
C		B	

K-map for EQ

A			
0	1	1	1
0	0	1	1
0	0	0	0
0	0	1	0
D			
C		B	

K-map for GT


$$LT = A' B' D + A' C + B' C D$$

$$EQ = A' B' C' D' + A' B C' D + A B C D + A B' C D' = (A \text{ xnor } C) \cdot (B \text{ xnor } D)$$

$$GT = B C' D' + A C' + A B D'$$

# Half Adder (1-bit)


---

 

A	B	S(um)	C(arry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



# Half Adder (1-bit)

 

A	B	S(um)	C(arry)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C = AB$$



# Full Adder

---

 

Cin	A	B	S(um)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Full Adder

Cin	AB			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$\begin{aligned}
 S &= \overline{\text{Cin}} \overline{A} \overline{B} + \overline{\text{Cin}} A \overline{B} + \text{Cin} A B + \text{Cin} \overline{A} \overline{B} \\
 &= \text{Cin} (\overline{A} \overline{B} + A \overline{B}) + \overline{\text{Cin}} (\overline{A} \overline{B} + A \overline{B}) \\
 &= \text{Cin} (\overline{A} \oplus B) + \overline{\text{Cin}} (A \oplus B) \\
 &= \text{Cin} \oplus A \oplus B
 \end{aligned}$$

Cin	AB			
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$\text{Cout} = \text{Cin} B + \text{Cin} A + AB$$

Or

Cin	AB			
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$\text{Cout} = AB + \text{Cin} (\overline{A} B + A \overline{B}) = AB + \text{Cin} (A \oplus B)$$

Cin	A	B	S(um)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1




# Full adder alternative circuit

# Constructing a Full Adder using Half Adders (cont.)

- Sum Boolean expression of a full adder:

$$\begin{aligned} \text{sum} &= a'b'c_{in} + a'bc_{in}' + ab'c_{in}' + abc_{in} \\ \text{sum} &= c_{in}(a'b' + ab) + c_{in}'(a'b + ab') \\ \text{sum} &= c_{in}(a \oplus b)' + c_{in}'(a \oplus b) \\ \text{sum} &= (a \oplus b) \oplus c \end{aligned}$$

 
- $C_{out}$  Boolean expression of a full adder:



$$\begin{aligned} C_{out} &= a'bc_{in} + ab'c_{in} \\ &\quad + abc_{in}' + abc_{in} \\ C_{out} &= ab + a'bc_{in} + ab'c_{in} \\ C_{out} &= ab + c_{in}(a'b + ab') \\ C_{out} &= ab + c_{in}(a \oplus b) \end{aligned}$$
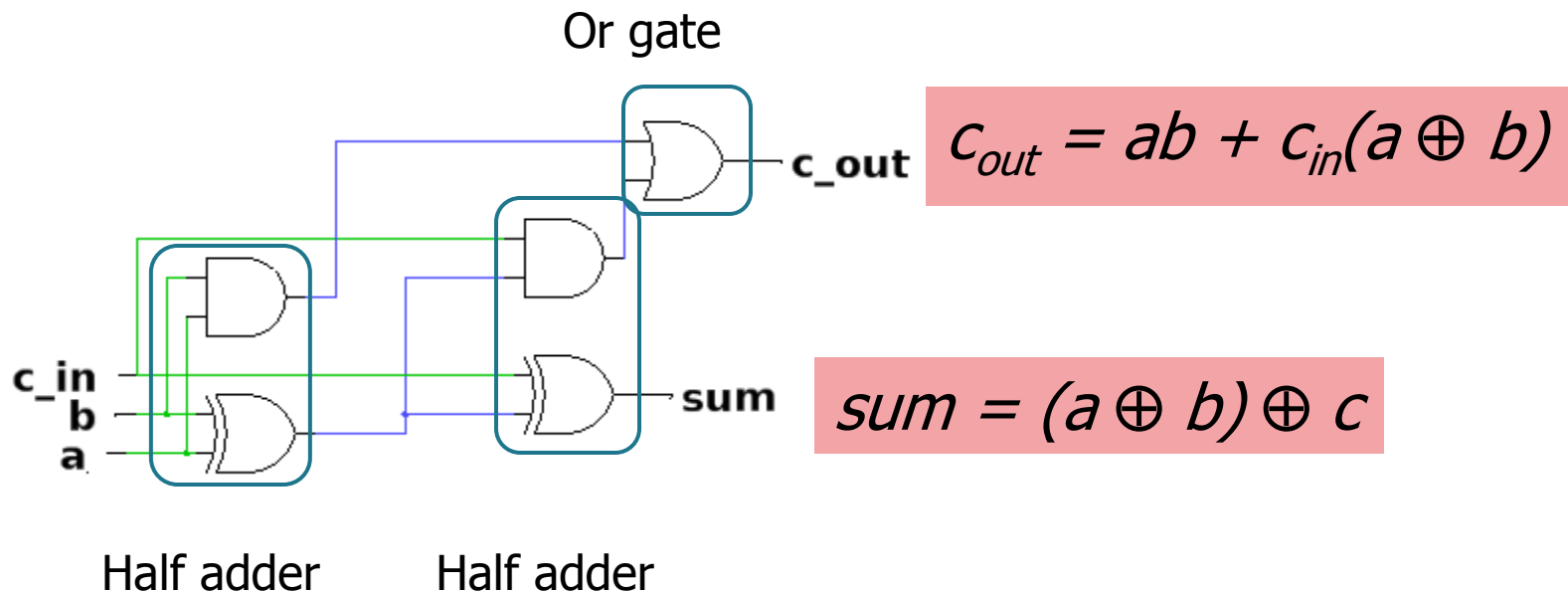
# Constructing a Full Adder using Half Adders (cont.)


- ▶ Circuit diagram of a full adder (which is made up of 2 half adders and 1 OR gate):



# Full Adder

$$S = C_{in} \oplus A \oplus B$$

$$C_{out} = AB + C_{in}(A \oplus B)$$

 


# Full Adder


---

$$S = \text{Cin} \oplus A \oplus B$$
 
$$\text{Cout} = AB + \text{Cin}(A \oplus B)$$




# 4-bit Ripple Adder using Full Adder

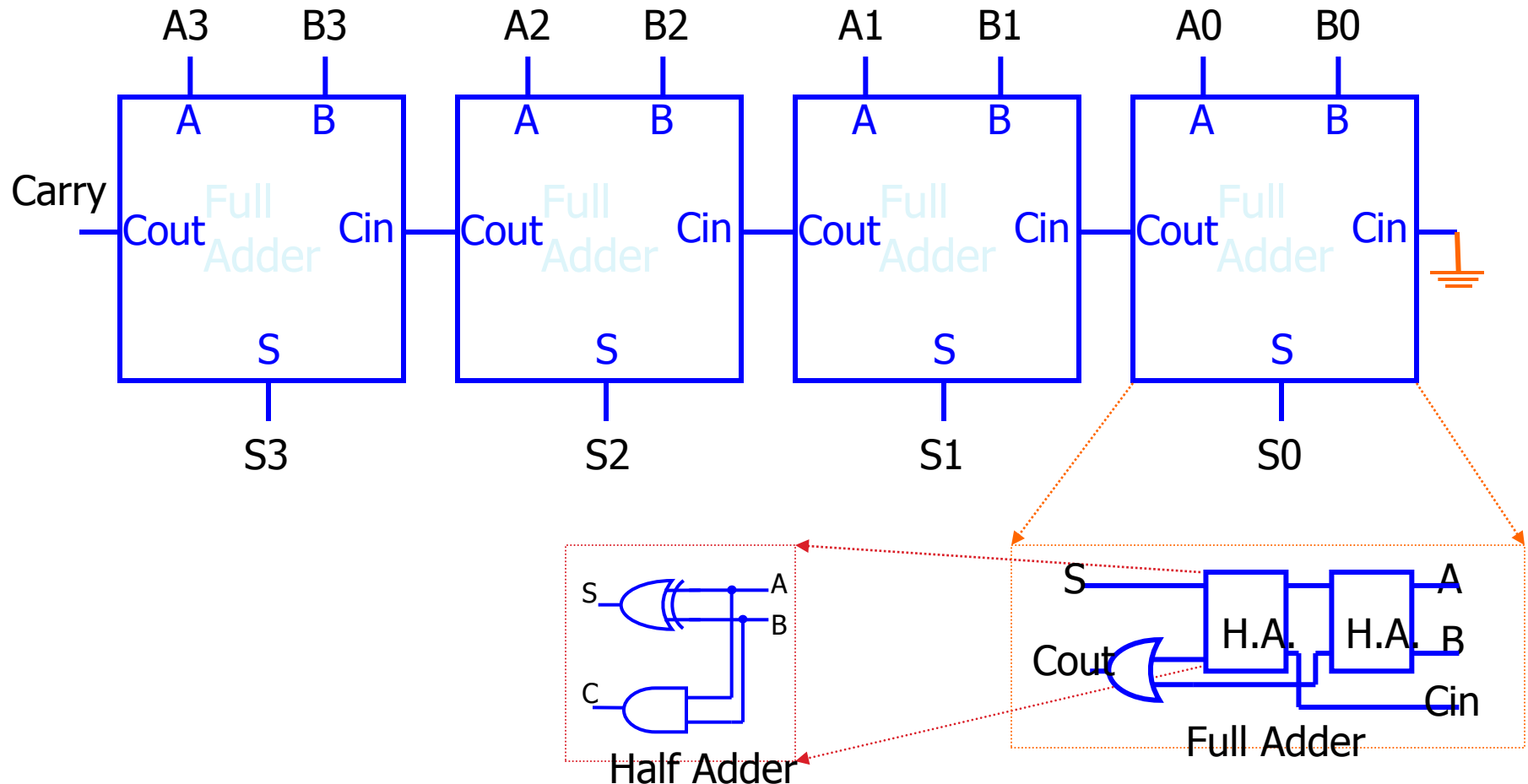

# Issue of 4-bit Ripple Adder

---

 

# Issue of Ripple Adder

---

- ▶ Carry propagation is the main issue in an N-bit ripple adder
- ▶ A faster adder needs to address the serial propagation of the carry bit
- ▶ Let's re-examine the equation for full adders





# Carry Generate & Propagate

---

$$C_{i+1} = A_i B_i + C_i (A_i + B_i)$$

$$g_i = A_i B_i \quad (\text{generate})$$

$$p_i = A_i + B_i \quad (\text{propagate})$$

$$C_{i+1} = g_i + p_i C_i$$

$$C_1 = g_0 + p_0 C_0$$


$$C_2 = g_1 + p_1 C_1 = g_1 + p_1 g_0 + p_1 p_0 C_0$$

$$C_3 = g_2 + p_2 C_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0$$

$$C_4 = g_3 + p_3 C_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$$


Note that all the carry's are only  
dependent on input A and B and C

# 4-bit Carry-Lookahead Adder (CLA)

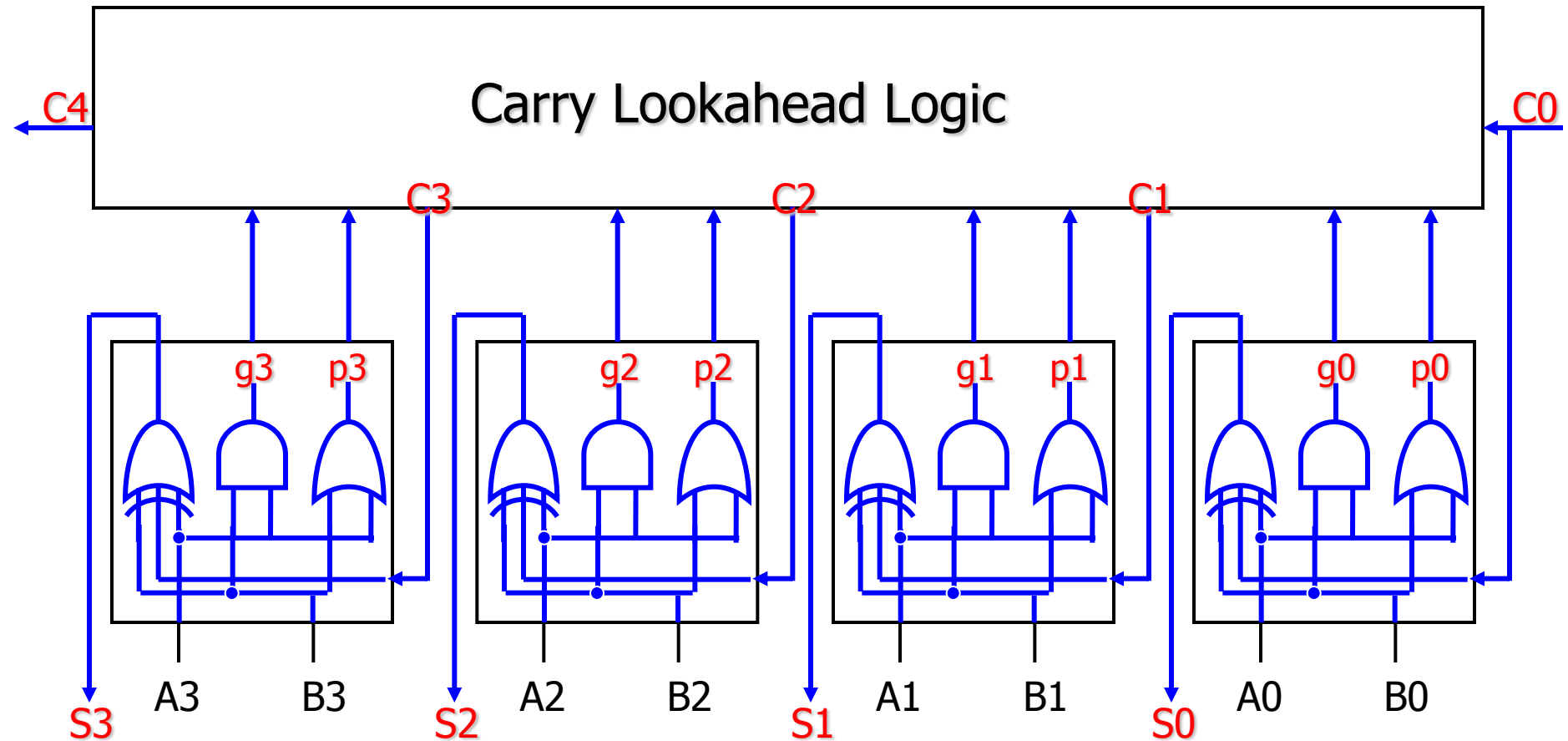

$$S_i = C_i \oplus A_i \oplus B_i$$
$$g_i = A_i B_i \quad (\text{generate})$$
$$p_i = A_i + B_i \quad (\text{propagate})$$
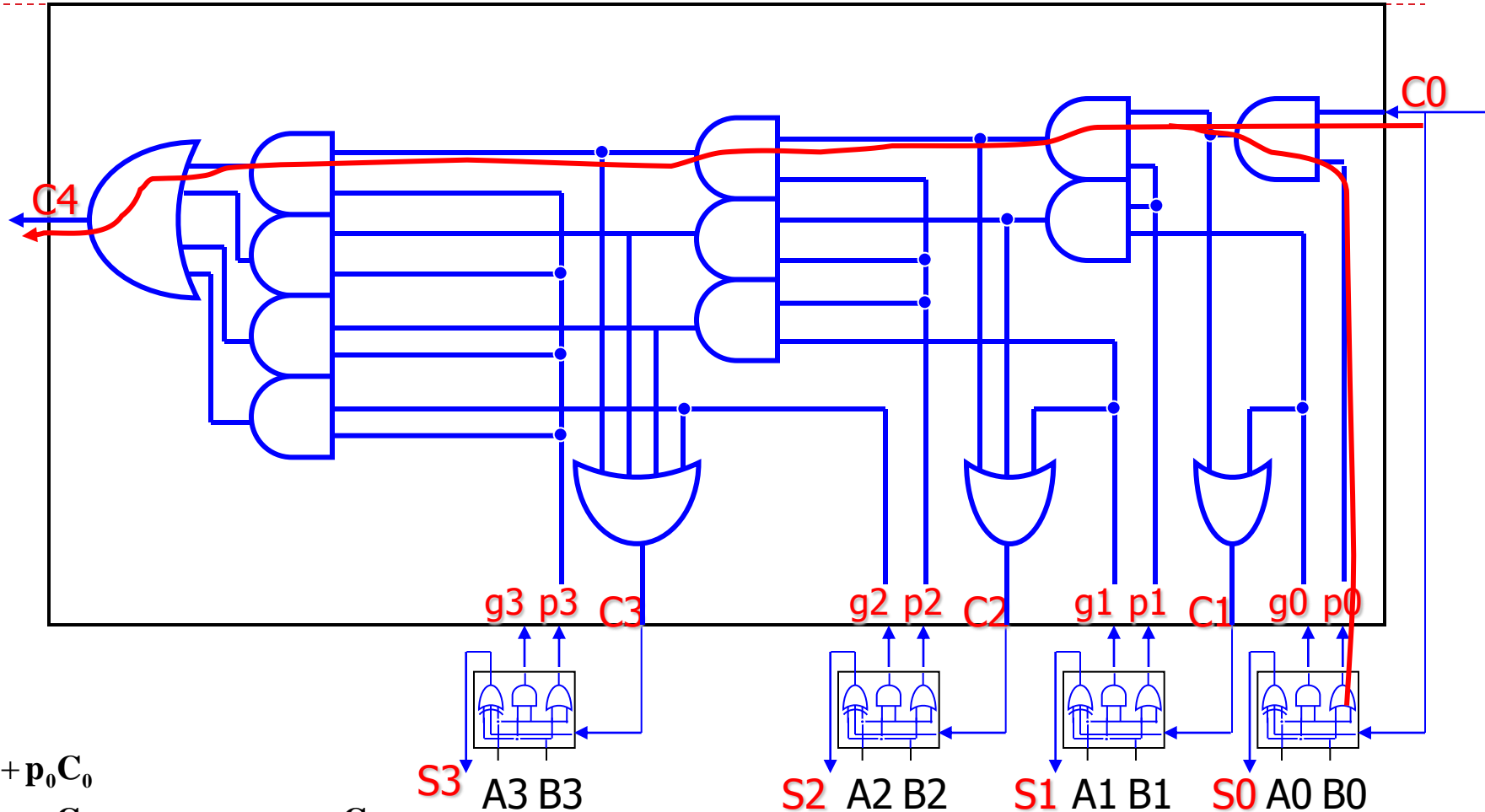
# Inefficient Implementation of Carry Lookahead Logic



$$C_1 = g_0 + p_0 C_0$$

$$C_2 = g_1 + p_1 C_1 = g_1 + p_1 g_0 + p_1 p_0 C_0$$

$$C_3 = g_2 + p_2 C_2$$

$$C_4 = g_3 + p_3 C_3$$


Reuse some gate output results →

Little Improvement

Carry Delay is  $4 \cdot D_{\text{AND}} + 2 \cdot D_{\text{OR}}$  for Carry  $C_4$

# Implementation of Carry Lookahead Logic

## Carry Lookahead Logic

 

$$C_1 = g_0 + p_0 C_0$$

$$C_2 = g_1 + p_1 C_1 = g_1 + p_1 g_0 + p_1 p_0 C_0$$

$$C_3 = g_2 + p_2 C_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0$$


$$C_4 = g_3 + p_3 C_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$$

Only 3 Gate Delay for each Carry  $C_i$   
 $= D_{AND} + 2 * D_{OR}$

4 Gate Delay for each Sum  $S_i$   
 $= D_{AND} + 2 * D_{OR} + D_{XOR}$
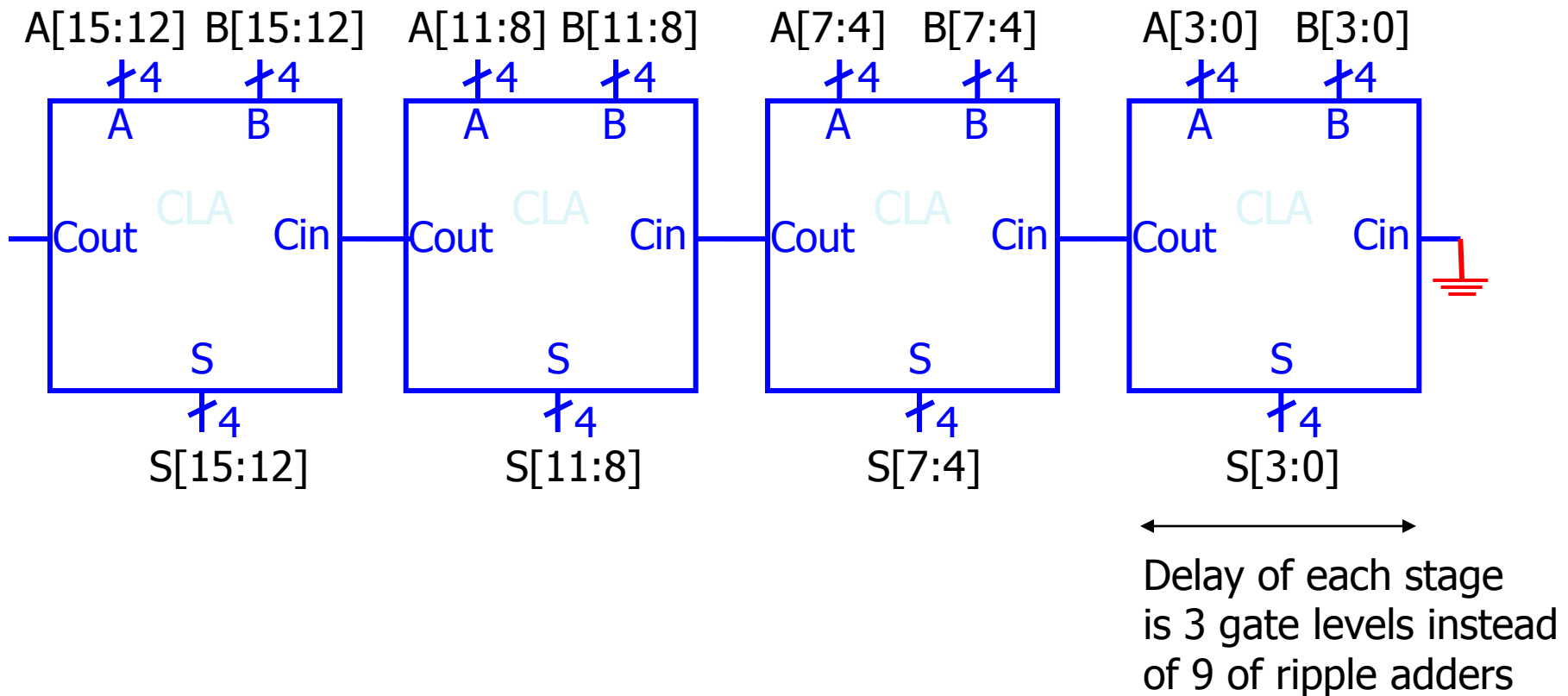
# Cascading CLA

- ▶ Similar to ripple adder, but different latency







# Unsigned Binary Multiply

$$\begin{array}{r} 101 \quad (5) \\ \times 111 \quad (7) \\ \hline 101 \\ 101 \\ 101 \\ \hline 100011 \quad (35) \end{array}$$




# Unsigned Integer Multiplier (2-bit)

2-bit by 2-bit

  

# N-to-M-Line Decoder ( $2^N \geq M$ )

---

 


A1	A0	D3	D2	D1	D0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0





# 2-to-4-Line Decoder

 

A1	A0	D3	D2	D1	D0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$D_0 = \overline{A_1} \overline{A_0}$$


$$D_1 = \overline{A_1} A_0$$

$$D_2 = A_1 \overline{A_0}$$

$$D_3 = A_1 A_0$$

How about if no one should be enabled ?

# 2-to-4-Line Decoder w/ Enable

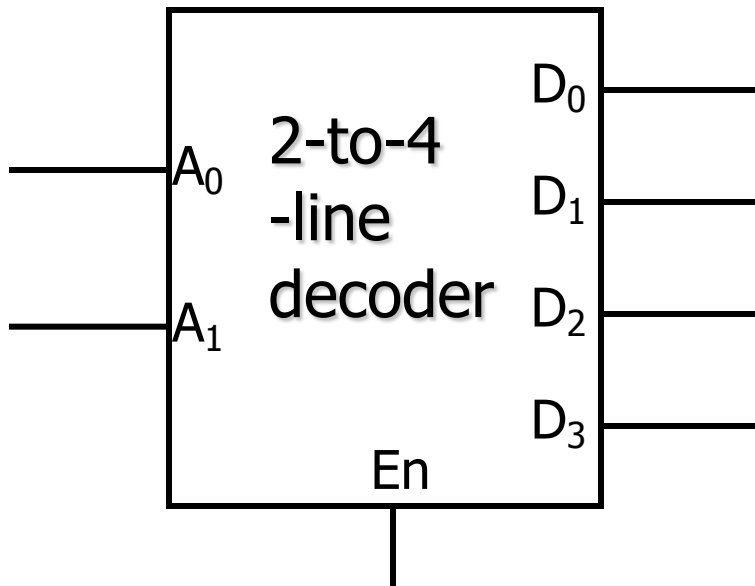

En	A1	A0	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0


$$D_0 = En \overline{A_1} \overline{A_0}$$

$$D_1 = En \overline{A_1} A_0$$

$$D_2 = En A_1 \overline{A_0}$$

$$D_3 = En A_1 A_0$$

# 2-to-4-Line Decoder w/ Enable

 

En	A1	A0	D3	D2	D1	D0
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

$$D_0 = \text{En} \overline{A_1} \overline{A_0}$$

$$D_1 = \text{En} \overline{A_1} A_0$$

$$D_2 = \text{En} A_1 \overline{A_0}$$

$$D_3 = \text{En} A_1 A_0$$



# 3-to-8-Line Decoder

---

Truth Table

A2	A1	A0	D 7	D 6	D 5	D 4	D 3	D 2	D 1	D 0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0



# 3-to-8-Line Decoder


---

Truth Table

A2	A1	A0	D 7	D 6	D 5	D 4	D 3	D 2	D 1	D 0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0



# 3-to-8-Line Decoder

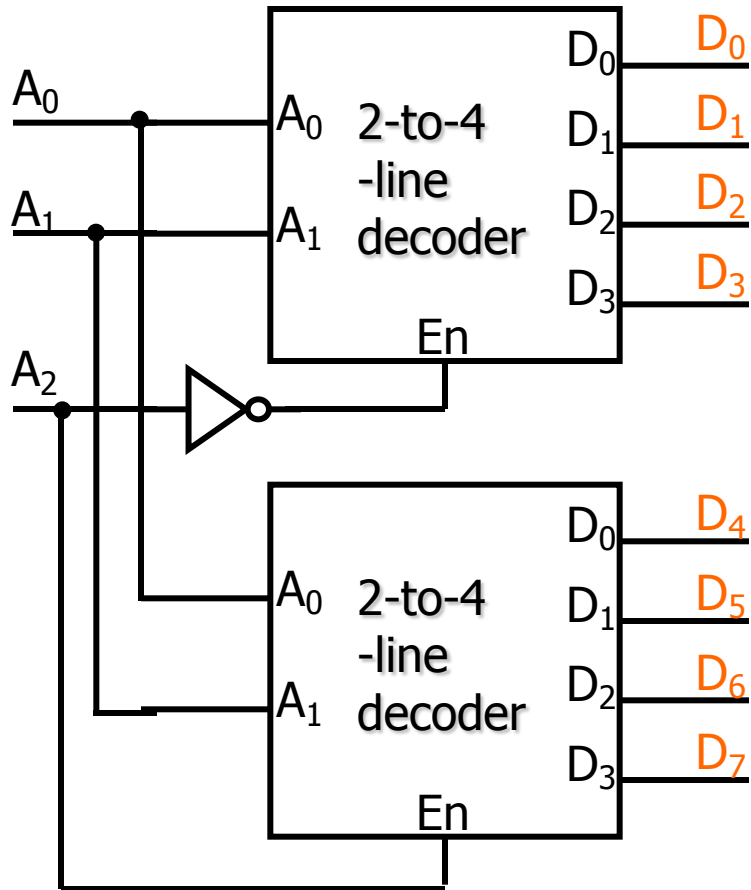


$A_2$	$A_1$	$A_0$	$D_7$	$D_6$	$D_5$	$D_4$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0



 
# Implementing Logic w/ Decoder

$$F1(X, Y, Z) = \sum m(1, 2, 6, 7)$$

$$F2(X, Y, Z) = \prod M(0, 1, 2, 3, 5, 7)$$



# Decoder as a Logic Building Block

 

**Decoder Generates Appropriate Minterm based on Control Signals**

**Example Function:**


$$F1 = A' B C' D + A' B' C D + A B C D$$

$$F2 = A B C' D' + A B C$$

$$F3 = (A' + B' + C' + D')$$




# Decoder as a Logic Building Block

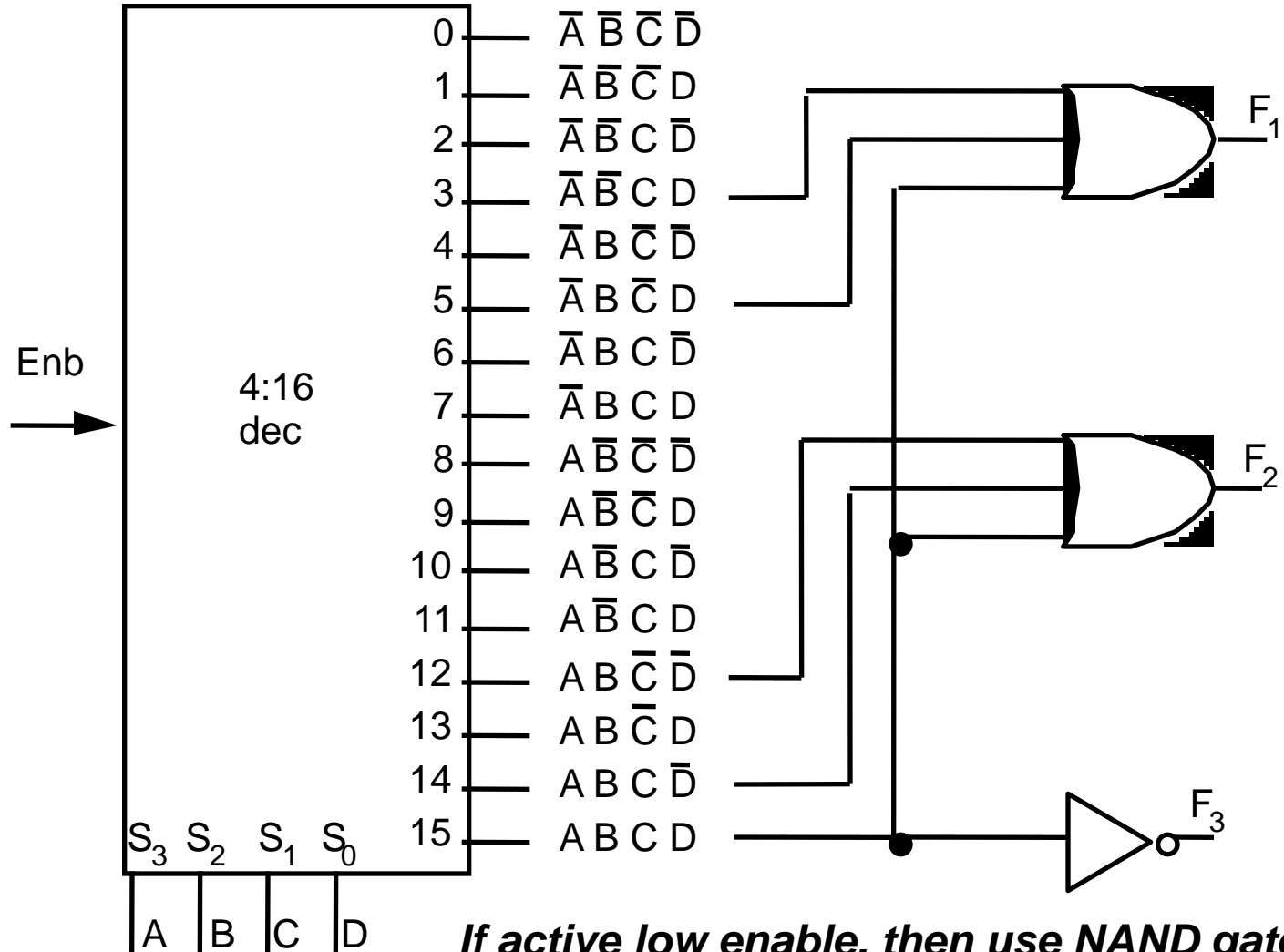

***If active low enable, then use NAND gates!***

# Multiplexers (Mux)


---

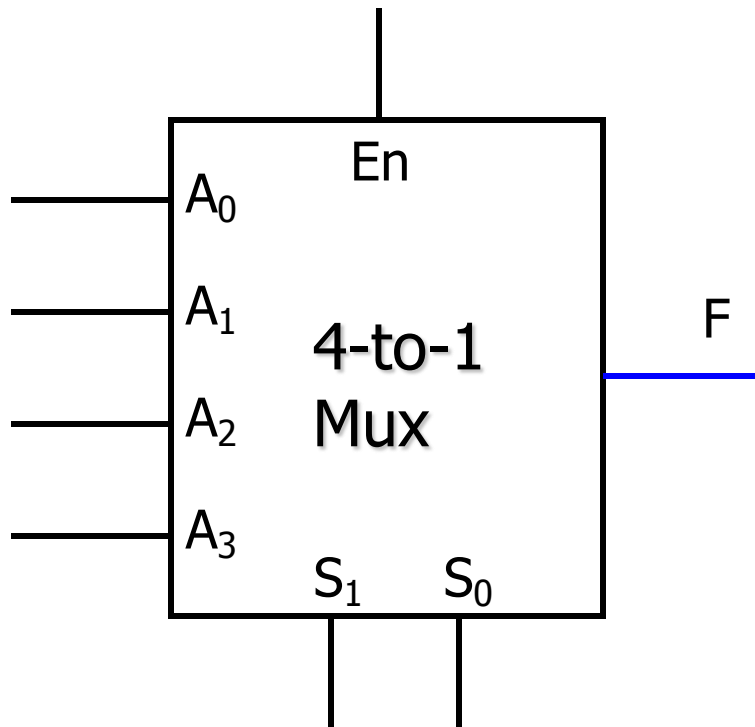

- ▶ **Functionality:** Selection of a particular input
- ▶ Route 1 of  $N$  inputs ( $A$ ) to the output  $F$
- ▶ Require  $\log_2^N$  selection bits ( $S$ )
- ▶ En(able) bit can disable the route and set  $F$  to 0

# Multiplexers (Mux) w/out Enable

---

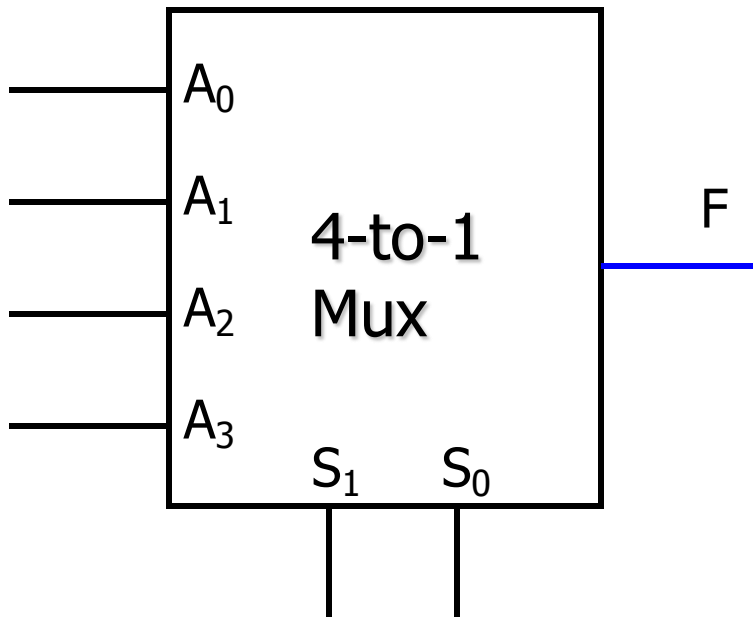


S1	S0	A3	A2	A1	A0	F
0	0	X	X	X	0	0
0	1	X	X	0	X	0
1	0	X	0	X	X	0
1	1	0	X	X	X	0
0	0	X	X	X	1	1
0	1	X	X	1	X	1
1	0	X	1	X	X	1
1	1	1	X	X	X	1



# Multiplexers (Mux) w/out Enable


---

 


$S_1$	$S_0$	$F$
0	0	$A_0$
0	1	$A_1$
1	0	$A_2$
1	1	$A_3$

$$F = \overline{S_1}\overline{S_0}A_0 + \overline{S_1}S_0A_1 + S_1\overline{S_0}A_2 + S_1S_0A_3$$

# Logic Diagram of a 4-to-1 Mux

 

# Multiplexers (Mux) w/ Enable

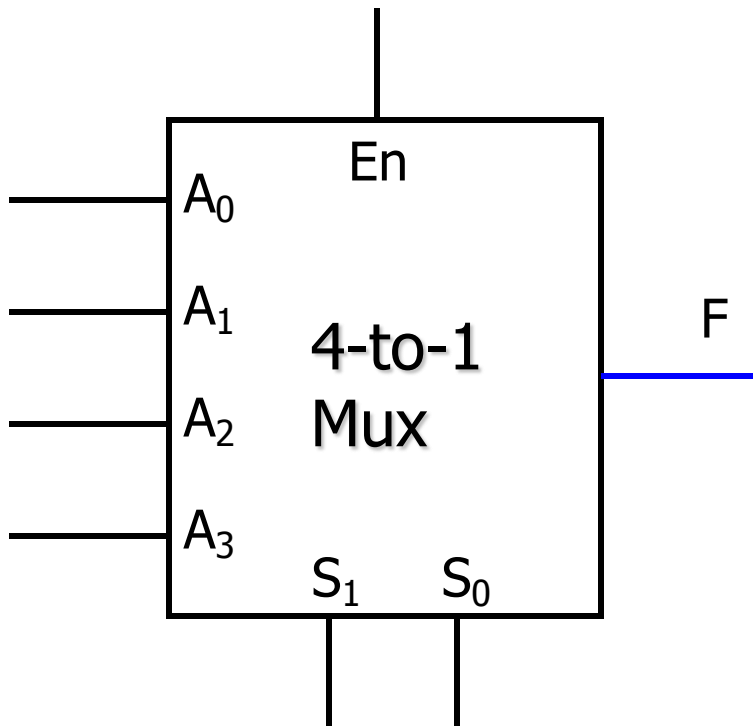


En	S1	S0	F
0	X	X	0
1	0	0	$A_0$
1	0	1	$A_1$
1	1	0	$A_2$
1	1	1	$A_3$

$$\begin{aligned} F &= En \cdot (\overline{S_1}\overline{S_0}A_0 + \overline{S_1}S_0A_1 + S_1\overline{S_0}A_2 + S_1S_0A_3) \\ &= En\overline{S_1}\overline{S_0}A_0 + En\overline{S_1}S_0A_1 + EnS_1\overline{S_0}A_2 + EnS_1S_0A_3 \end{aligned}$$


 
## 4-to-1 Mux w/ Enable Logic

$$F = E_n \cdot (\overline{S_1}\overline{S_0}A_0 + \overline{S_1}S_0A_1 + S_1\overline{S_0}A_2 + S_1S_0A_3)$$




# Design Canonical Form w/ MUX

$$F(A,B,C) = \overline{A}BC + A\overline{B}C + A\overline{B}\overline{C} + ABC$$

$$F(A,B,C) = \sum m(1, 2, 6, 7)$$

Each input in a MUX is a minterm

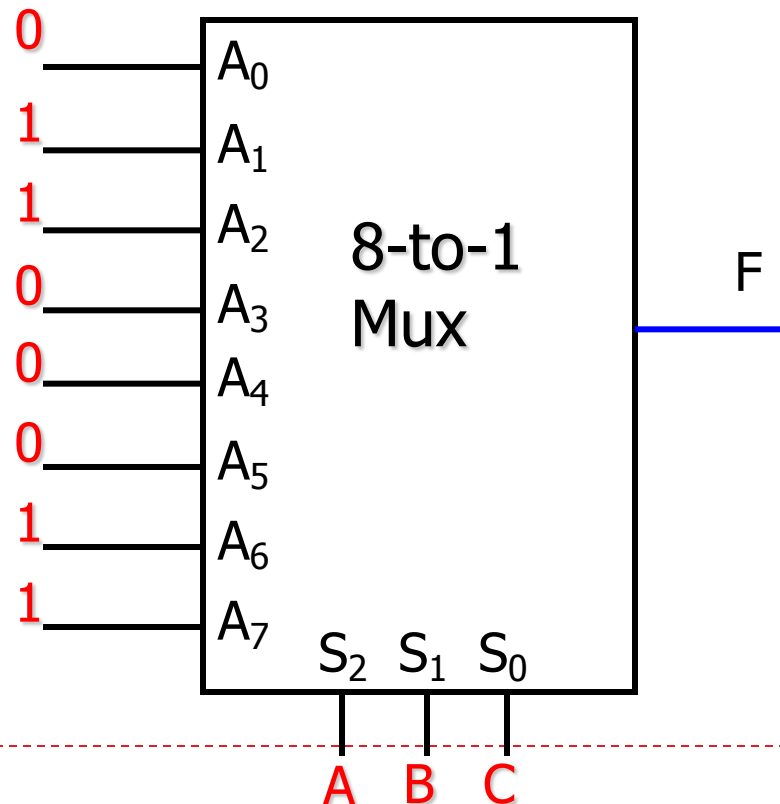



# Design Canonical Form w/ MUX

---

$$F(A,B,C) = \sum m(1, 2, 6, 7)$$

$$F = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$


A	B	F
0	0	
0	1	
1	0	
1	1	


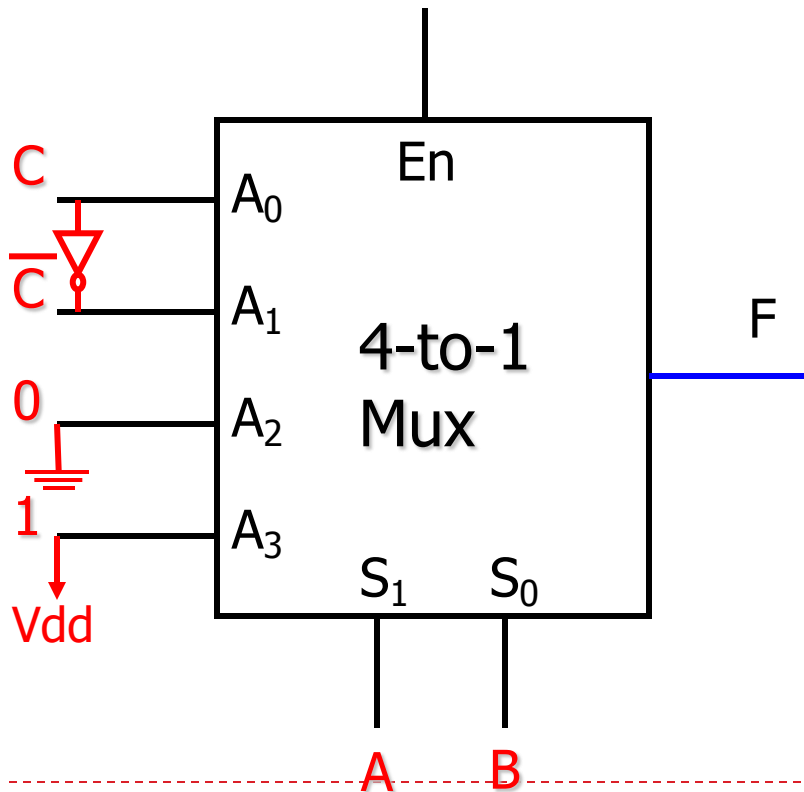
# Design Canonical Form w/ MUX

$$F = \sum m(1, 2, 6, 7)$$

$$F = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$




A	B	F
0	0	C
0	1	$\overline{C}$
1	0	0
1	1	1
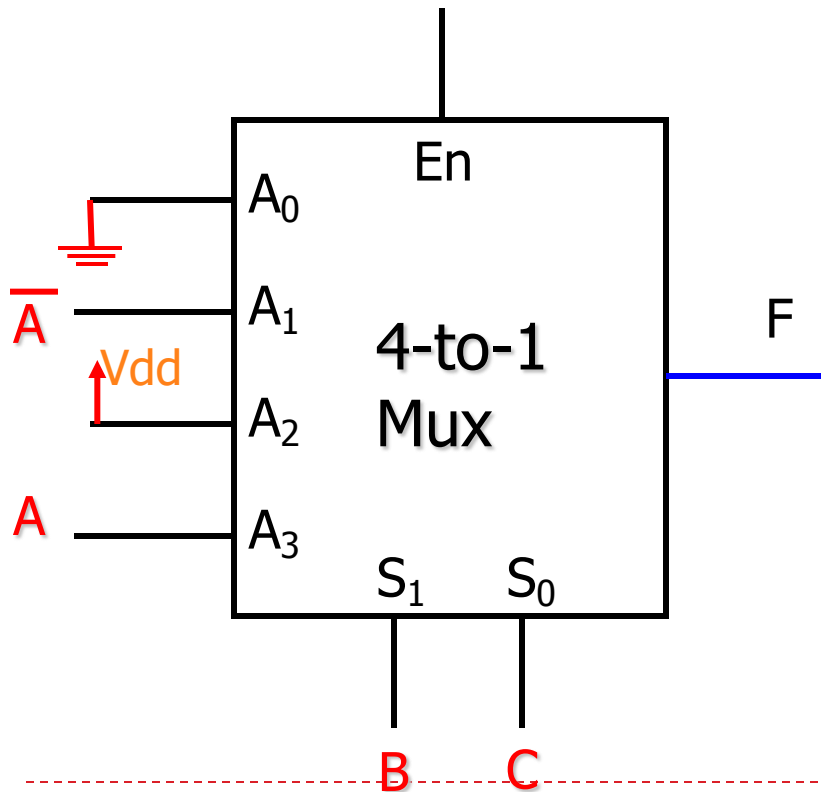
# Design Canonical Form w/ MUX

$$F = \sum m(1, 2, 6, 7)$$

$$F = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$



B	C	F
0	0	0
0	1	$\overline{A}$
1	0	1
1	1	A

# Implement a function using MUX

A combinational circuit is specified by the following Boolean function:

$$F(A,B,C,D) = \Sigma(0,2,6,7,8)$$


Implement the circuit using ONE 4:1 multiplexer and other necessary gates. Use A and B as MUX selection inputs. Only uncomplemented inputs are available.

Ans.  $F = A'B'C'D' + A'B'CD' + A'BCD' + A'BCD + AB'C'D'$

$$F = A[B'C'D'] + A'[B'C'D' + B'CD' + BCD' + BCD]$$


$$F = A[B(0) + B'(C'D')] + A'[B(CD' + CD) + B'(C'D' + CD')]$$
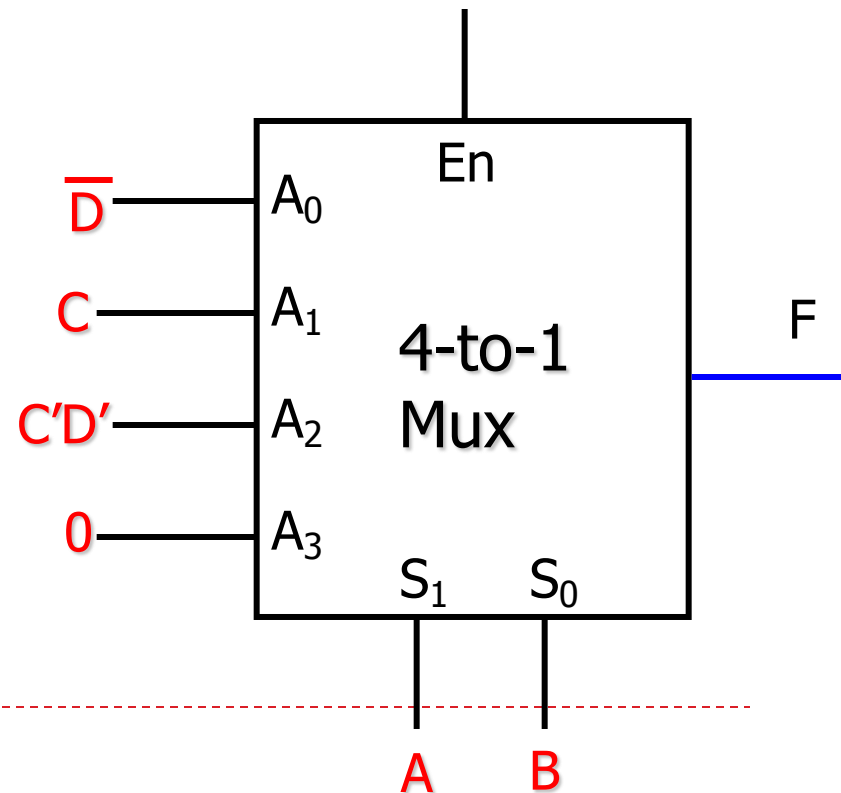
$$F = A[B(0) + B'(C'D')] + A'[B(C) + B'(D')]$$


 
# Design of Large Multiplexers


Large multiplexers can be implemented by cascaded smaller ones




Control signals  $B$  and  $C$  simultaneously choose one of  $I_0$ - $I_3$  and  $I_4$ - $I_7$

Control signal  $A$  chooses which of the upper or lower MUX's output to gate to  $Z$

## Alternative 8:1 Mux Implementation

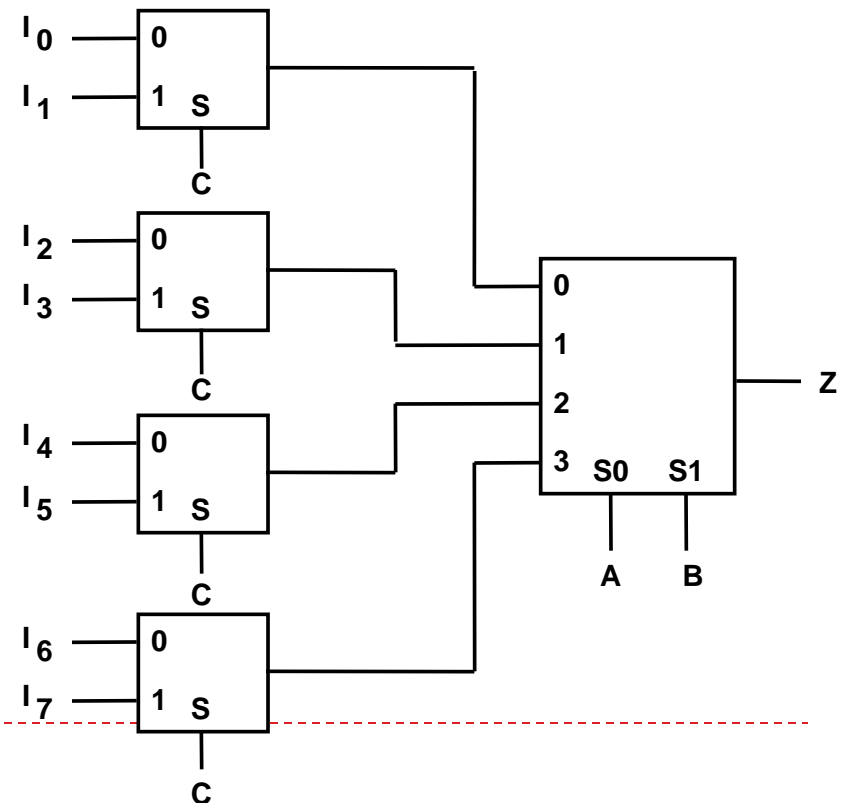


 - Large multiplexers can be made by cascading smaller ones



control signals B and C simultaneously choose one of I0, I1, I2, I3 and one of I4, I5, I6, I7

 control signal A chooses which of the upper or lower mux's output to gate to Z



# Multiplexers/Selectors as General Purpose Blocks


$2^{n-1}:1$  multiplexer can implement any function of  $n$  variables

$n-1$  control variables; remaining variable is a data input to the mux

 *Example:*  $F(A,B,C) = m_0 + m_2 + m_6 + m_7$


$$= A' B' C' + A' B C' + A B C' + A B C$$

$$= A' B' (C') + A' B (C') + A B' (0) + A B (1)$$



"Lookup Table"

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

- Realize  $F = B'CD' + ABC'$  with a 4:1 multiplexer and a minimum of other gates:


A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

0 when  $B'C'$

$D'$  when  $B'C$

A when  $BC'$

0 when  $BC$

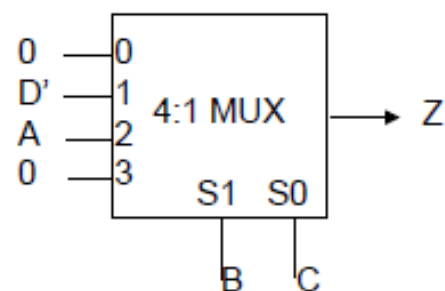

$$Z = B'C'(0) + B'C(D') + BC'(A) + BC(0)$$